


→ Objective :- Discuss the working of NAND gate with the help of circuit diagram and truth table

⇒ NAND GATE :- The NAND gate has an output that is normally at logic level "1" and only goes "Low" to logic level "0" when all of its inputs are logic level "1".

⇒ Diagram :-



NAND gate Equivalence :-

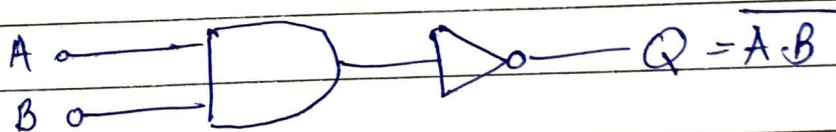

⇒ Truth table of NAND Gate

truth table		
B	A	Q
0	0	1
0	1	1
1	0	1
1	1	0

Read as A and B gives NOT Q

→ Working of NAND Gate :- It is just the reverse of AND gate like AND gate a NAND gate can be more than two inputs, like 3, 4, input NAND gate.

if both the input of nand gate are "0" then the result will be "1", or if both the input of nand gate are "1" then the result will be "0".

If one input is 0 and the other input is 1 it will give 1 as an output.

Advantage of NAND gate :-

- NAND gates are cost effective device and they have more storage capacity as per their size.
- High endurance and durability

Disadvantage of NAND gate :-

- When compared with the NOR gate, the NAND memory architecture and speed are less reliable.