

NAME:- Priyanki Verma  
Course:- MCA  
Sem:- 1st  
Sec:- B  
Roll.No:- 2101147  
Student Id:- 217/2029


Priyanki

Q-1) Discuss the working of NAND gate with the help of circuit diagram and truth table.

Ans- Working:- A NAND gate ("not AND gate") is a logic gate that produces a low output (0) only if all its inputs are true, and high output (1) otherwise.

- Hence the NAND gate is the inverse of an AND gate, and its circuit is produced by connecting an AND gate to a NOT gate.
- Just like an AND gate, a NAND gate may have any number of input probes but only one output probe.
- The NAND gate performs the logical NAND operation.
- NAND gates are known as universal gates, which means they are a type of logic gate which can implement any Boolean function without the need to use any other gate type.
- The symbol of a NAND gate is similar to the AND gate, but a bubble is drawn at the output point of the AND gate.

Circuit Diagram :-

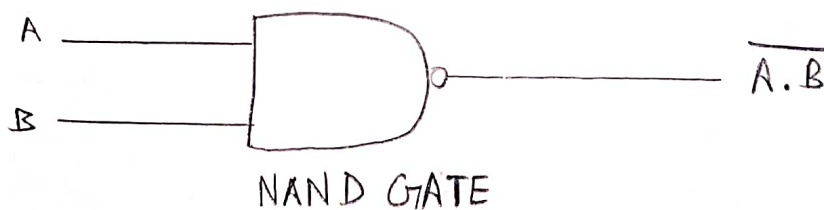

# Truth Table :-

AND

NAND

Input		Output	Output
A	B	$X = A \cdot B$	$X = \overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0