

Name - Pankaj Kumar
 University Roll no. - 2101138
 Section - D
 Student Id - 21711269


Q-1 Nand Gate :-

The NAND gate is a combination of ~~and~~ an AND gate and NOT gate. They are connected in cascade form. It is also called Negated And gate.

The NAND gate provides the false or low output only when their outputs is high or true. The NAND gate is essential because it different types of boolean function are implemented by using it. The NAND gate has the property of functional completeness by using the

The function completeness means any types of gate can be implemented by using the NAND gate. It performs the function of OR, NOR and AND gate.

The logic circuit of the NAND gate is :

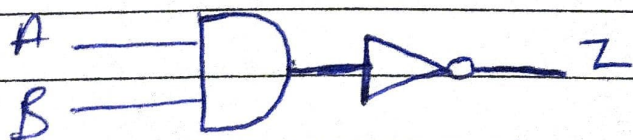

$$Z = \overline{A \cdot B}$$

Pankaj

Name - Pankaj Rawat
 University Roll no. 2101188
 Student Id = 21711269

The equation is read as "Z equals NOT A AND B". Since the logic circuit involves an AND gate followed by an inverter. The output can only be low when both the inputs are high.

The Truth table of NAND Gate

A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

From the truth table of the NAND gate it is clear that all the inputs must be high to get a low output and if any of the input is low the output obtained will be high. If any of the input is high the output will be high that is 1.

Pankaj