

Name- Salvi Gushin


Course- MCA I "A"

Roll no- 63(21712095)


Computer organisation practice GPBC-102,103).

Ans1. Nand gate - the Nand gate is a special type of logic gate in the logic circuit.

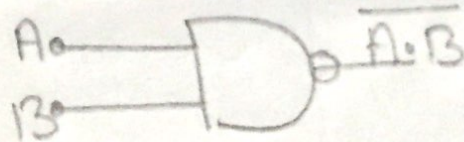- The Nand gate is universal gate. means all basic gates such as AND, OR and NOT gate can be constructed using NAND gate.
- The Nand gate is combination of NOT-AND gate.



⇒ Nand gate

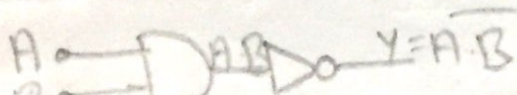

⇒ 2 Input AND + NOT gate

• Truth Table -


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

- In this, Nand gate, there are two input value and a single output value.
- There are $2^2=4$ possible combination of outputs.
- The logic or Boolean expression for Nand gate is the complement of logic multiplication of inputs denoted by a full stop or a single dot, as $(A \cdot B)' = Y$.
- The value of Y will be true when any one of the inputs is set to 0.

3-input Nand gate-

⇒ 3 input gate has 3 input.

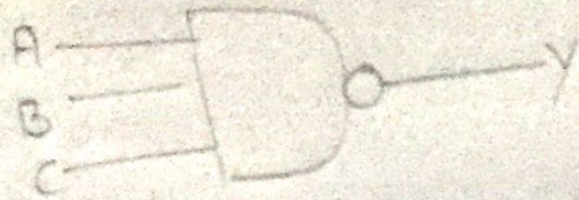- the Nand gate can be cascaded together to form any number of individual inputs.
- There are $2^3=8$ possible combination of inputs



⇒ 3-Input NAND gate.

Truth Table

A	B	C	Output (Y)
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

*

*

*