

NAME: RAJAT RAWAT
DATE: 22-03-22
UNIVERSITY ROLL NO: 2101162
ENROLLMENT NOS: PV-2101162
COURSE: MCA
SECTION: B
STUDENT ID: 21711179
SUBJECT: Computer Organization Practical

Ans NAND Gate: In digital electronics, a NAND gate is combination of NOT-AND gate, which produces an output which is false only if all its inputs are true.

The NAND gate is significant because any Boolean function can be implemented by using a combination of NAND gates. This property is called functional completeness.

NAND gate using circuit diagram


APPARATUS: The logic NAND gate IC, power supply, hookup wires, breadboard.

THEORY: The logic gate is generally classed as a universal gate. All gates can be implemented by NAND gate.


Boolean expression $\Rightarrow Q = \overline{A \cdot B}$

NAND gate has an output low (0) only when its inputs are high (1)

Circuit diagram

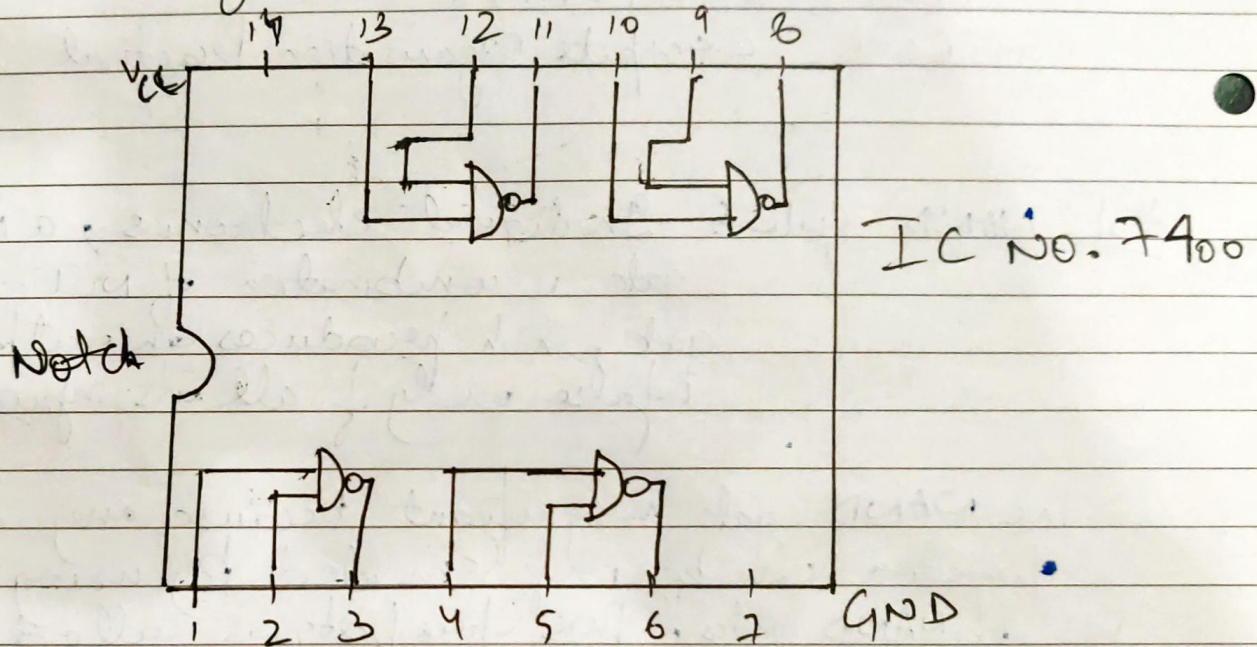

Logic Diagram

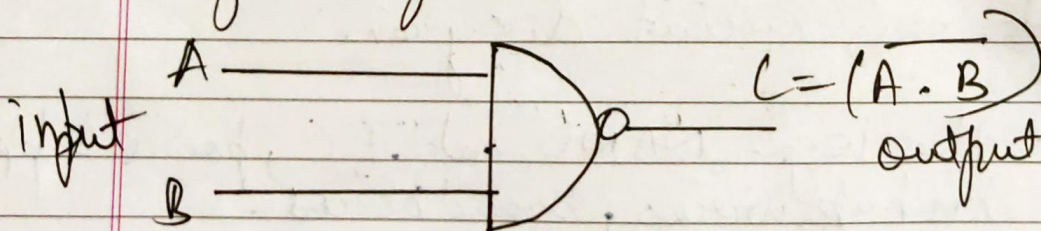

Truth Table

A	B	C ($\overline{A \cdot B}$)
0	0	1
0	1	1
1	0	1
1	1	0